

# Building an ALU (Part 1):

# Today's lecture

- **We start building our computer!**
  - We'll start with the arithmetic/logic unit (ALU)
- **Adding single bits**
  - Half Adders and Full Adder
- **Multi-bit Arithmetic**
  - Hierarchical design
  - Subtraction
- **Building a Logic Unit**
  - Multiplexors

# Arithmetic Logic Units (ALUs)


- The **computation** in a computer processor takes place in the **arithmetic logic unit**. This unit performs:
  - Arithmetic operations
    - e.g., addition and subtraction
  - Bit-wise logical operations
    - e.g., AND, OR, NOT, XOR
- Typically these operations are performed on multi-bit words
  - The MIPS-subset processor we will build uses 32-bit words

*In Lab 3 you will build a 32-bit ALU with the above operations*

# Binary Addition Review


|   |   |   |   |   |   |         |
|---|---|---|---|---|---|---------|
|   | 1 | 1 | 1 | 0 |   | Carries |
|   |   | 1 | 0 | 1 | 1 | Augend  |
| + |   | 1 | 1 | 1 | 0 | Addend  |
|   | 1 | 1 | 0 | 0 | 1 | Sum     |

# First Bit Position

 

# First Bit Position's Truth Table


| X | Y | C | S |
|---|---|---|---|
| 0 | 0 |   |   |
| 0 | 1 |   |   |
| 1 | 0 |   |   |
| 1 | 1 |   |   |

 

# Half Adder

- Adds two input bits to produce a sum and carry out.

| X | Y | C | S |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

 

$$C = XY$$

$$S = X'Y + XY'$$


$$= X \oplus Y$$

XOR

- *carry out is worth twice as much as the sum bit*

# Second Bit Position

- (and every subsequent position)

 



# Second Bit Position's Truth Table

- Adding 3 bits together to get a two bit number


0 + 0 + 0 = 00  
0 + 0 + 1 = 01  
0 + 1 + 0 = 01  
0 + 1 + 1 = 10  
1 + 0 + 0 = 01  
1 + 0 + 1 = 10  
1 + 1 + 0 = 10  
1 + 1 + 1 = 11

| X | Y | C <sub>in</sub> | C <sub>out</sub> | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0               | 0                | 0 |
| 0 | 0 | 1               | 0                | 1 |
| 0 | 1 | 0               | 0                | 1 |
| 0 | 1 | 1               | 1                | 0 |
| 1 | 0 | 0               | 0                | 1 |
| 1 | 0 | 1               | 1                | 0 |
| 1 | 1 | 0               | 1                | 0 |
| 1 | 1 | 1               | 1                | 1 |
 
# Full Adder

- Adds three input bits to produce a sum and carry out.

$$S = X \oplus Y \oplus C_{in}$$
$$C_{out} = XY + (X \oplus Y)C_{in}$$



| X | Y | C <sub>in</sub> | C <sub>out</sub> | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0               | 0                | 0 |
| 0 | 0 | 1               | 0                | 1 |
| 0 | 1 | 0               | 0                | 1 |
| 0 | 1 | 1               | 1                | 0 |
| 1 | 0 | 0               | 0                | 1 |
| 1 | 0 | 1               | 1                | 0 |
| 1 | 1 | 0               | 1                | 0 |
| 1 | 1 | 1               | 1                | 1 |

# Full Adder Circuit


- A Full Adder can be built with two half adders

$$S = X \oplus Y \oplus C_{in}$$
$$C_{out} = XY + (X \oplus Y)C_{in}$$

Half Adder Equations

$$C = XY$$

$$S = X \oplus Y$$

 


# Building multi-bit adders

- Recall our discussion about hierarchical design
  - *(The stop lights to prevent train collisions...)*
- We're going to build multi-bit adders by chaining full adders


$$\begin{array}{r} \text{CO} \quad C_3 \quad C_2 \quad C_1 \quad \text{Carries} \\ A_3 \quad A_2 \quad A_1 \quad A_0 \quad \text{Augend} \\ + \quad B_3 \quad B_2 \quad B_1 \quad B_0 \quad \text{Addend} \\ \hline S_3 \quad S_2 \quad S_1 \quad S_0 \quad \text{Sum} \end{array}$$

- Example: 4-bit adder

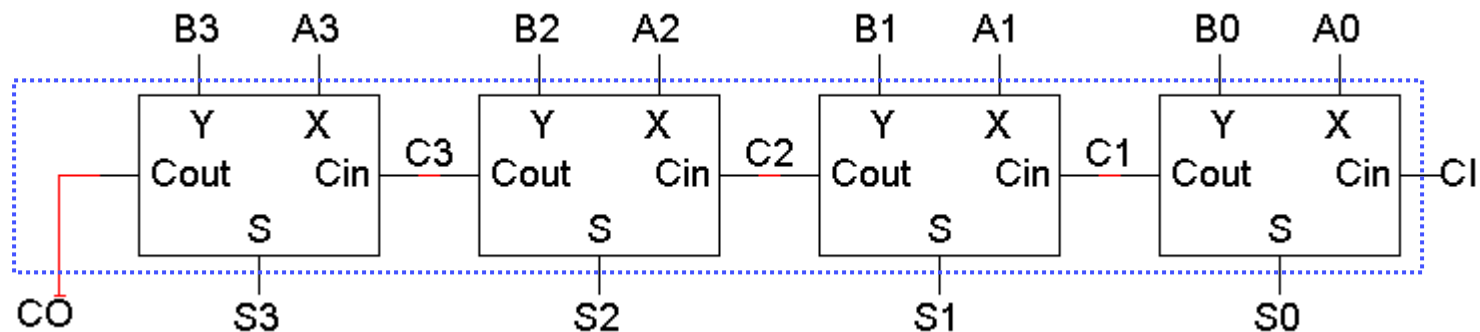

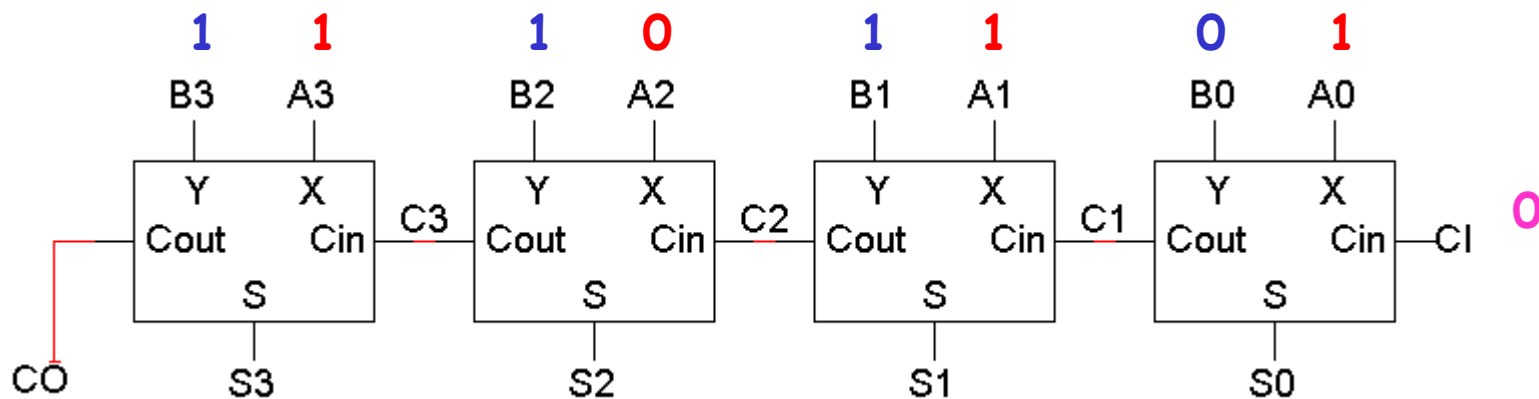
# An example of 4-bit addition

- Let's try our initial example: A=1011 (eleven), B=1110 (fourteen).


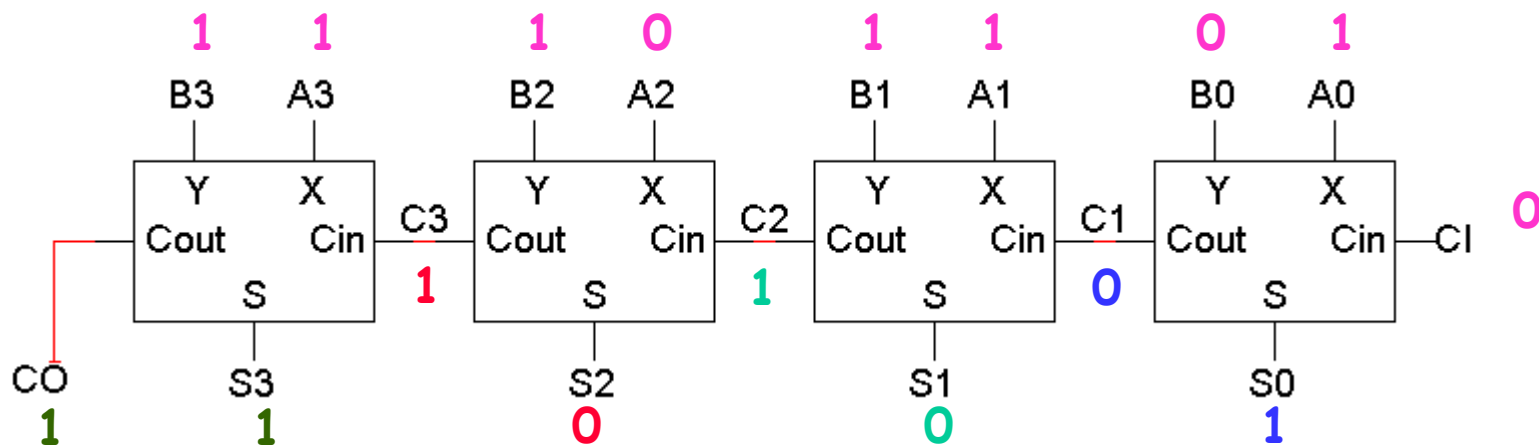
# An example of 4-bit addition

- Let's try our initial example: A=1011 (eleven), B=1110 (fourteen).



1. Fill in all the inputs, including  $C_i=0$
2. The circuit produces  $C_1$  and  $S_0$  ( $1 + 0 + 0 = 01$ )
3. Use  $C_1$  to find  $C_2$  and  $S_1$  ( $1 + 1 + 0 = 10$ )
4. Use  $C_2$  to compute  $C_3$  and  $S_2$  ( $0 + 1 + 1 = 10$ )
5. Use  $C_3$  to compute  $C_0$  and  $S_3$  ( $1 + 1 + 1 = 11$ )

Woohoo! The final answer is 11001 (twenty-five) *if we consider it a 5-bit output.*

# Implementing Subtraction

- We said last time that we implement subtraction
  - By negating the second input and then adding

$$A - B = A + (-B)$$


- Negating in 2's complement is
  - Inverting the bits and adding one

$$-B = \sim B + 1$$

- Substituting in:

$$A - B = A + (-B) =$$

# Implementing Subtraction, cont.

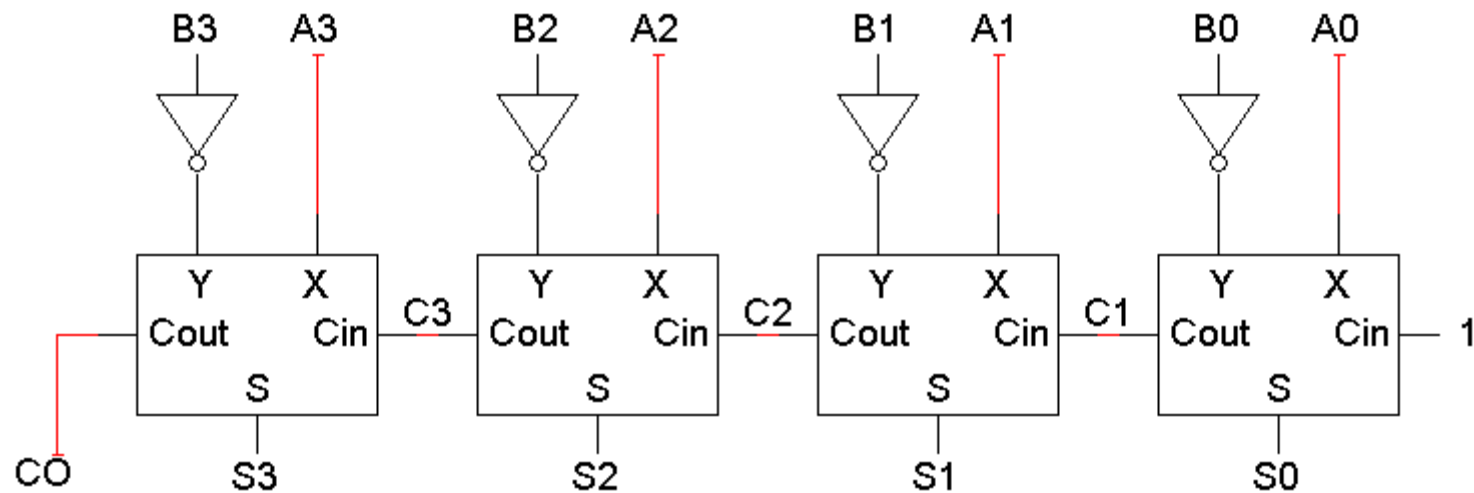




# Addition + Subtraction in one circuit

- XOR gates let us selectively complement the B input.

$$X \oplus 0 = X$$

$$X \oplus 1 = X'$$

 - When **Sub** = 0,  $Y = B$  and  $C_{in} = 0$ . Result =  $A + B + 0 = A + B$ .
- When **Sub** = 1,  $Y = \sim B$  and  $C_{in} = 1$ . Result =  $A + \sim B + 1 = A - B$ .



# Data vs. Control

- We'll delineate two groups of signals in the hardware
- Datapath
  - *These generally carry the numbers we're crunching*
  - *E.g., the X and Y inputs and the output S*
- Control
  - *These generally control how data flows and what operations are performed*
  - *E.g., the SUB signal.*

# Logical Operations

- In addition to ADD and SUBTRACT, we want our ALU to perform bit-wise AND, OR, NOT, and XOR.
- This should be straight forward.
  - We have gates that perform each of these operations.

X

Y

# Selecting the desired logical operation

- We need a control signal to specify the desired operation:

- We'll call that sign R
- 4 operations means R is 2 bits

| $R_1$ | $R_0$ | Output                 |
|-------|-------|------------------------|
| 0     | 0     | $G_i = X_i Y_i$        |
| 0     | 1     | $G_i = X_i + Y_i$      |
| 1     | 0     | $G_i = X_i'$           |
| 1     | 1     | $G_i = X_i \oplus Y_i$ |


AND

OR

NOR

XOR

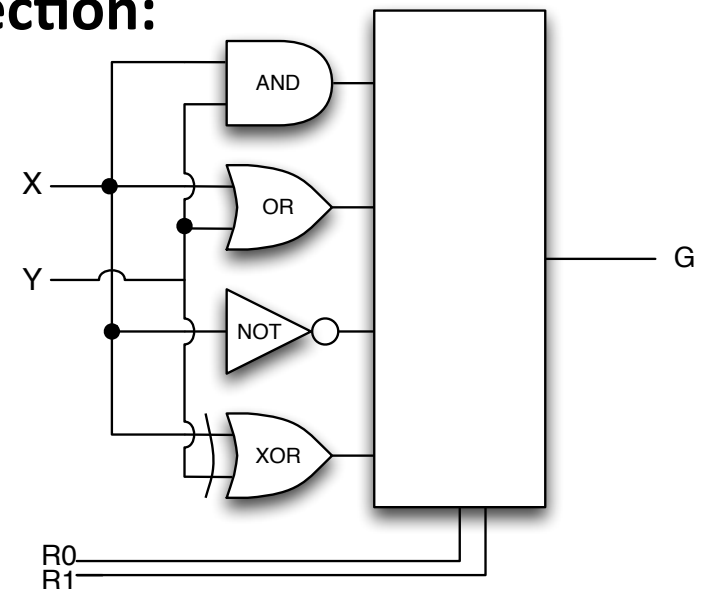- We need a circuit to perform the selection:




# Multiplexors

- A multiplexor is a circuit that (logically) selects one of its inputs to connect to its output

- Consider a 2-to-1 multiplexor. It has:

 - 2 data inputs ( $I_0, I_1$ )
- a 1-bit control input ( $S$ )
- 1 data output ( $Y$ )



| S | Y     |
|---|-------|
| 0 | $I_0$ |
| 1 | $I_1$ |


- The control input selects which data input is output:

$$Y = S' I_0 + S I_1$$

# Multiplexors, cont.

- In general, a multiplexor (mux) has:
  - $2^N$  data inputs ( $I_0 - I_{2^N-1}$ )
  - an  $N$ -bit control input ( $S$ )
  - 1 data output ( $Y$ )
- If  $S = K$  then  $Y = I_K$
- Examples:
  - 4-to-1 mux: 4 data inputs, 2-bit control input
    - $Y = S_0'S_1'I_0 + S_0S_1'I_1 + S_0'S_1I_2 + S_0S_1I_3$
  - 16-to-1 mux: 16 data inputs, 4-bit control input

# Complete 1-bit Logic Unit

 

| $R_1$ | $R_0$ | Output                 |
|-------|-------|------------------------|
| 0     | 0     | $G_i = X_i Y_i$        |
| 0     | 1     | $G_i = X_i + Y_i$      |
| 1     | 0     | $G_i = X_i'$           |
| 1     | 1     | $G_i = X_i \oplus Y_i$ |