





Registers and Register Files

Today's lecture

- **More D Flip flops**
 - Asynchronous reset
 - Enable
- **Random Access Memory (RAM)**
 - Addressable storage
- **Register Files**
 - Registers
 - Decoders

Flip flop with asynchronous reset

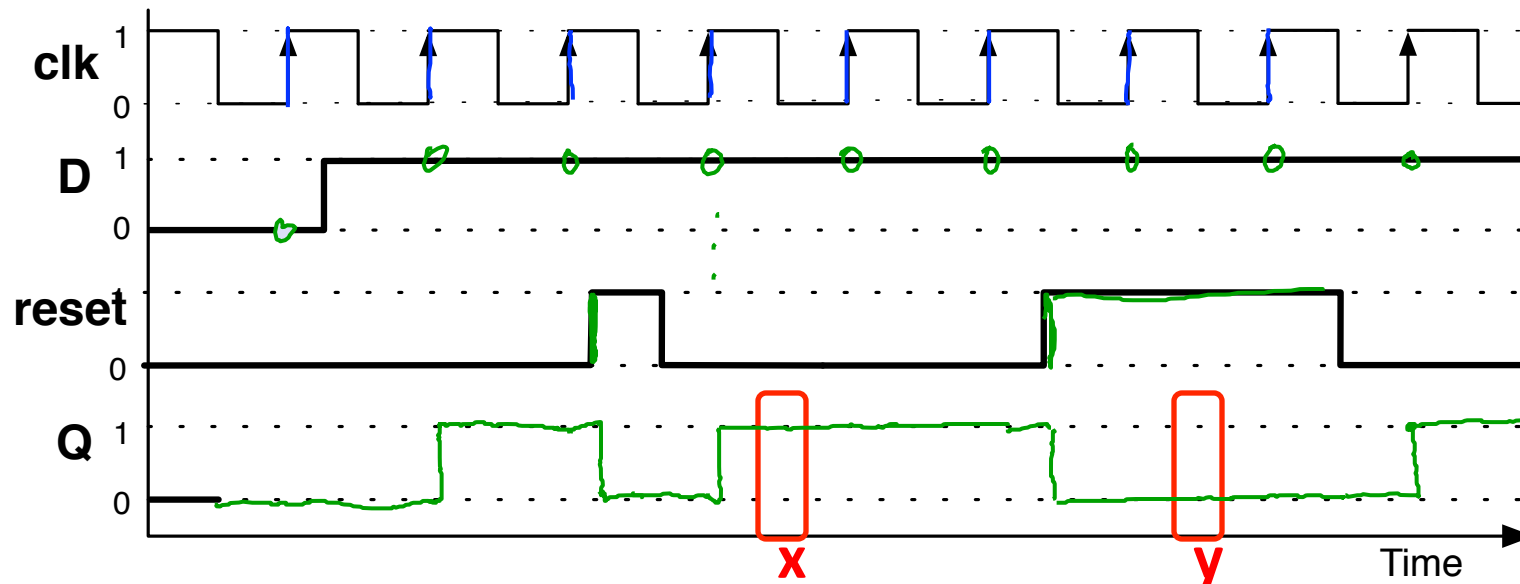 
- **Asynchronous** = pertaining to operation without the use of fixed time intervals (opposed to synchronous).
 - Processed immediately, ignores clock.
- Reset = set the value to zero



x,y =
a) 0,0
b) 0,1
c) 1,0
d) 1,1

Asynchronous Reset implementation

One example possible implementation

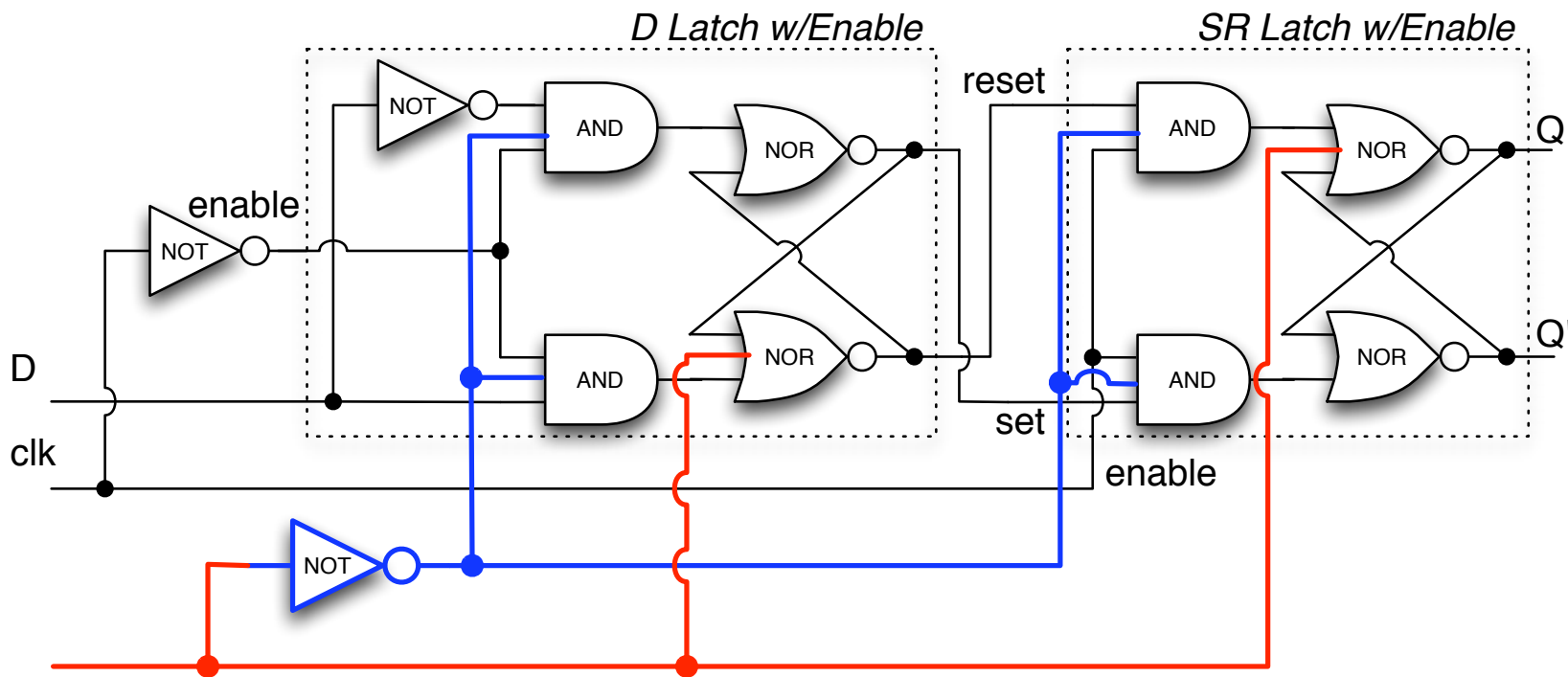



Ignores inputs and current state.

Forces Q output to zero.

(Not required material)

Flip flop with enable

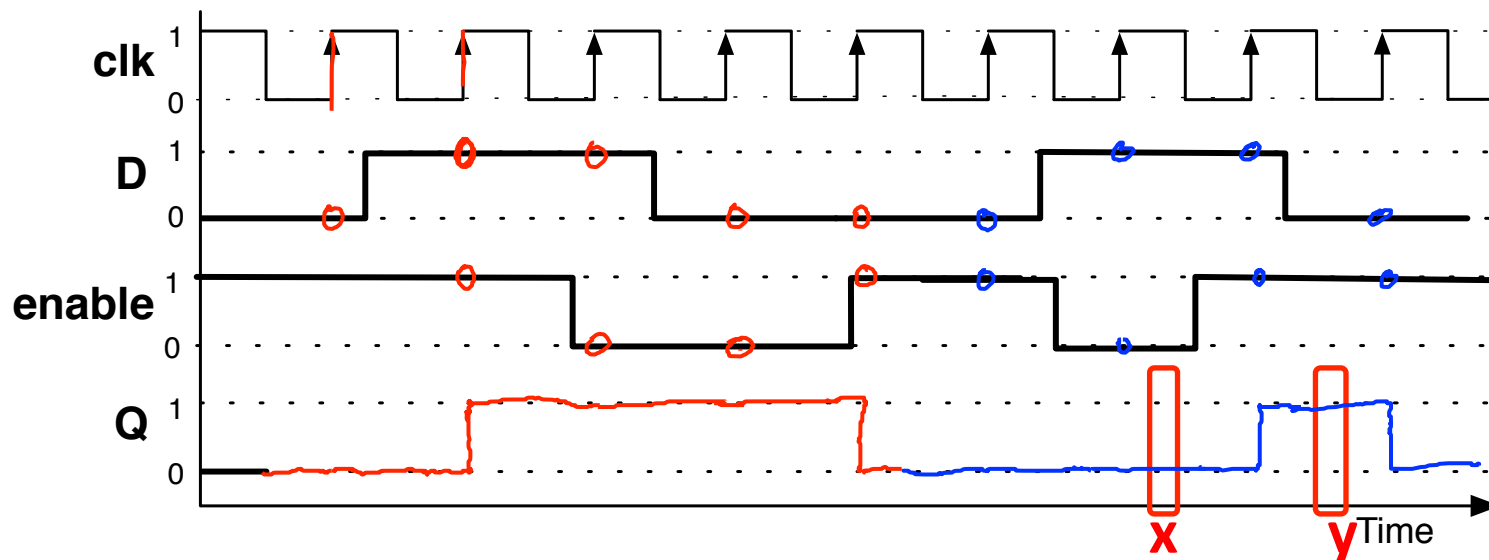 - When enable=0, Q output doesn't change on rising edge
 - Behaves normally when enable=1





x,y =
a) 0,0
b) 0,1
c) 1,0
d) 1,1

How can we store more than 1 bit?

4b - register

  - We build registers out of flip flops.
 - Example **4-bit register** made of **four D flip flops**
 - 1 data input, 1 data output per flip flop
 - All control signals use the same input



Introduction to RAM

- To provide lots of storage we use Random-access memory, or **RAM**.
- Remember the basic capabilities of a memory:
 - It should be able to store a value.
 - You should be able to read the value that was saved.
 - You should be able to change the stored value.
- A RAM is similar, except that it can store many values.
 - An address will specify which memory value we're interested in.
 - Each value can be a multiple-bit word (e.g., 32 bits).
- We'll refine the memory properties as follows:

A RAM should be able to:

- Store many words, one per address
- Read the word that was saved at a particular address
- Change the word that's saved at a particular address

A picture of memory

- You can think of memory as being an array of data.
 - The address serves as an array index.
 - A k -bit address can specify one of 2^k words
 - Each address refers to one word of data.
 - Each word can store N bits

$2^k \times N$ memory

- You can read or modify the data at any given memory address, just like you can read or modify the contents of an array at any given index.
 - This is what “random access” means.

Address	<u>Data</u>
00000000	
00000001	
00000002	
.	
.	
.	
.	
.	
.	
.	
.	
.	
.	
FFFFFFFFD	
FFFFFFFE	
FFFFFFF	

$k \rightarrow N \text{ bits} \rightarrow$

Random Access Memory


8

Register File: a special kind of memory

- We'll focus first on a special kind of RAM: a register file
- Our register file will have:
 - 2 read ports, so we can read two values simultaneously
 - 1 write port

- This will allow us to:

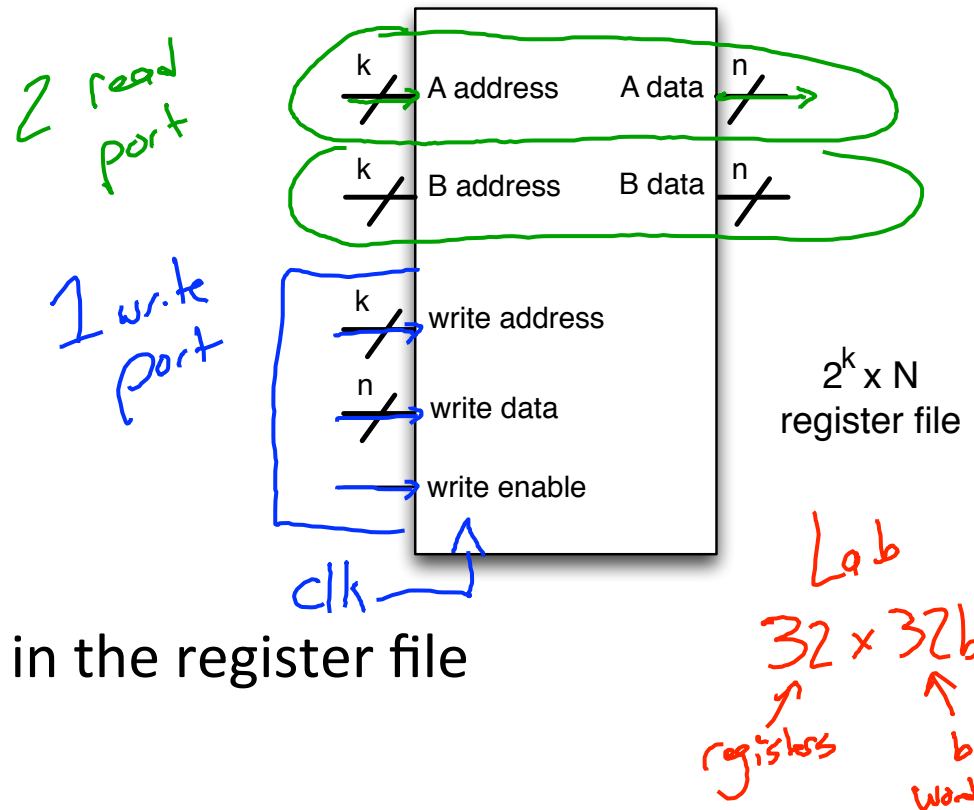
- Read 2 numbers
- Add them together
- Store the result back in the register file



Register file implementation


- A register file has 3 parts
 - The Storage: An array of registers
 - The Read Ports: Output the value of selected register
 - The Write Port: Selectively write one of the registers

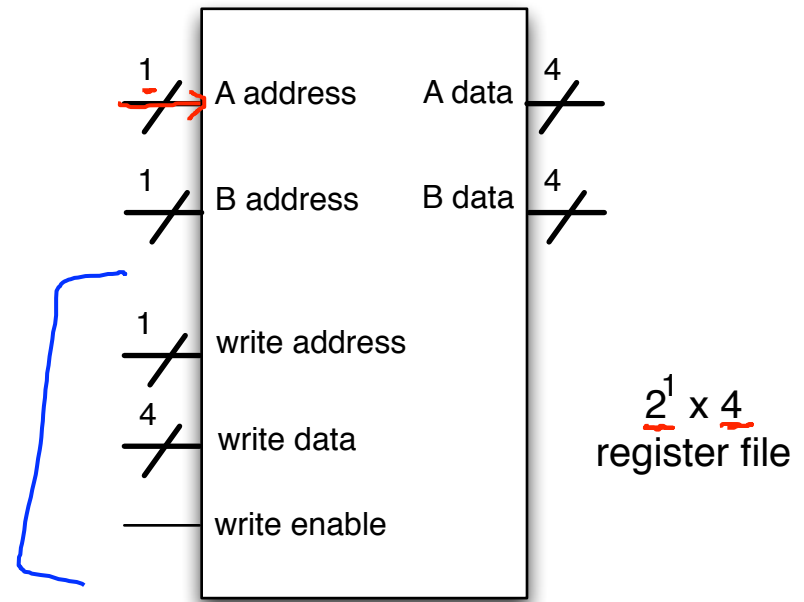- Let's consider a 2 word memory
 - with 4-bit words



Step 1: Allocating the storage

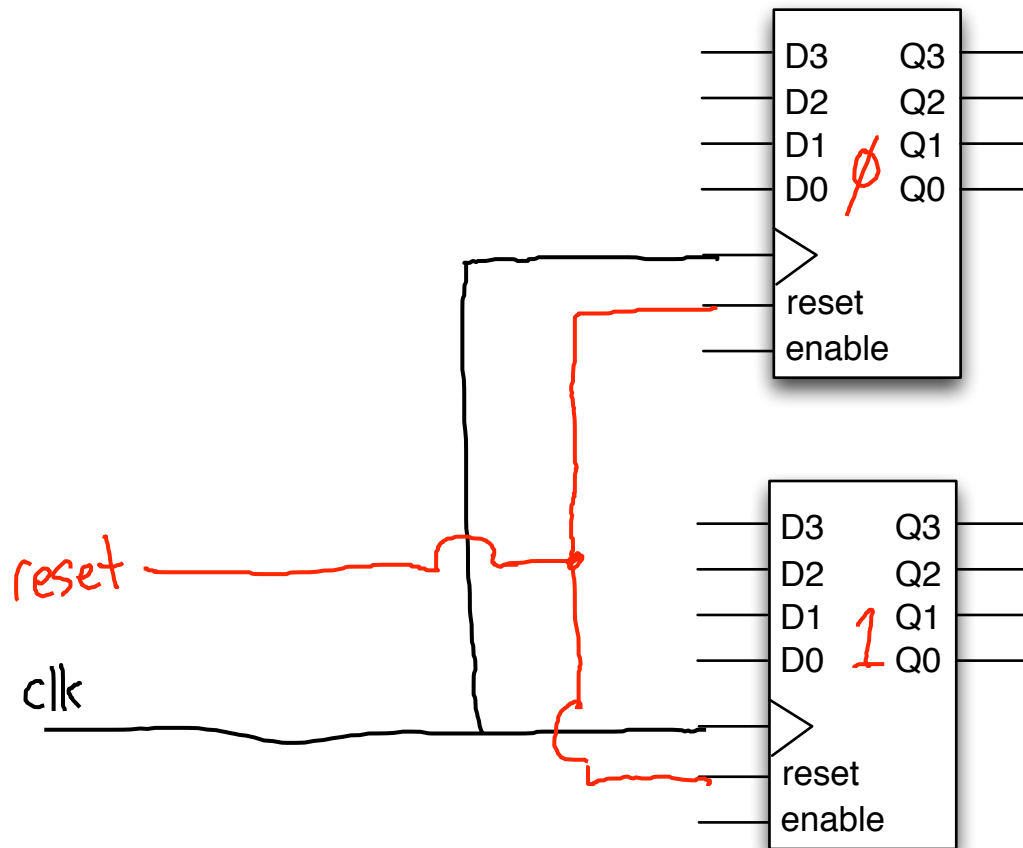
- We need two 4-bit registers
 - We'll wire their clocks and resets together



Step 2: Implementing the read ports

- The read address (1 bit) specifies which register to read.


A address

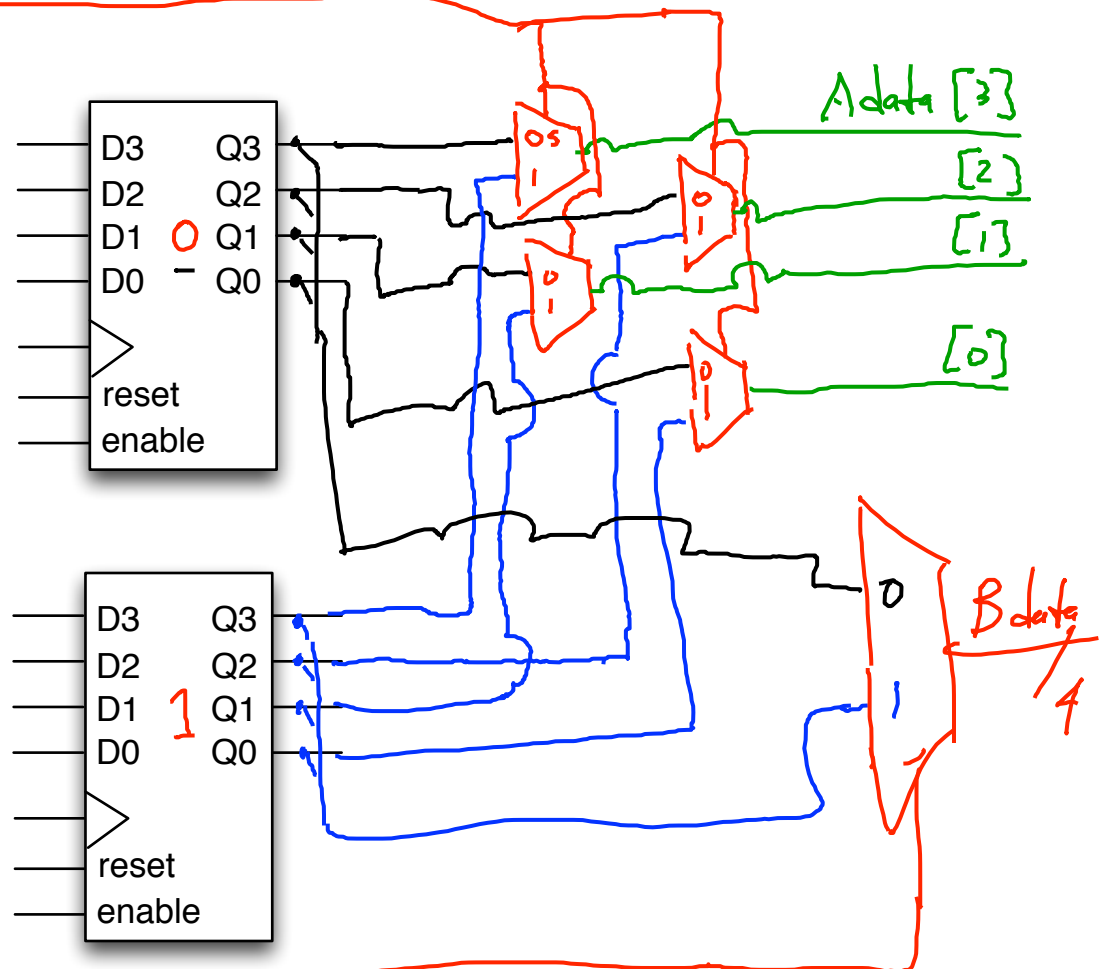

B address



Step 3: Implementing the write ports

 - The write address (1 bit) specifies which register to write.



Decoders

  
- This circuit is a 1-to-2 decoder
 - It decodes a 1-bit address, setting the specified output to 1
 - Assuming the circuit is enabled




EN	S0	(Q1,Q0)
0	X	(0, 0)
1	0	(0, 1)
1	1	(1, 0)

Scaling Decoders

 - Decoders can be generalized as follows
- A n-to-2ⁿ decoder:
 - Has a 1-bit enable input, and an n-bit select input
 - Has 2ⁿ outputs
 - All the outputs are zero, except the selectth if enable = 1
 - If enable = 0, all outputs are zero.
- A 2-to-4 decoder:



EN	S[1:0]	Q[3:0]
0	X	(0,0,0,0)
1	(0,0)	(0,0,0,1)
1	<u>(0,1)</u>	(0,0,1,0)
1	(1,0)	(0,1,0,0)
1	(1,1)	(1,0,0,0)

 


EN	S[4:0]	Q[31:0]
0	X	0x0000
1	0	0x0001
1	1	0x0002
1
1	30	0x4000
1	31	0x8000


Register file implementation

- A register file has 3 parts
 - **The Storage**: An array of registers
 - **The Read Ports**: Output the value of selected register
 - **The Write Port**: Selectively write one of the registers

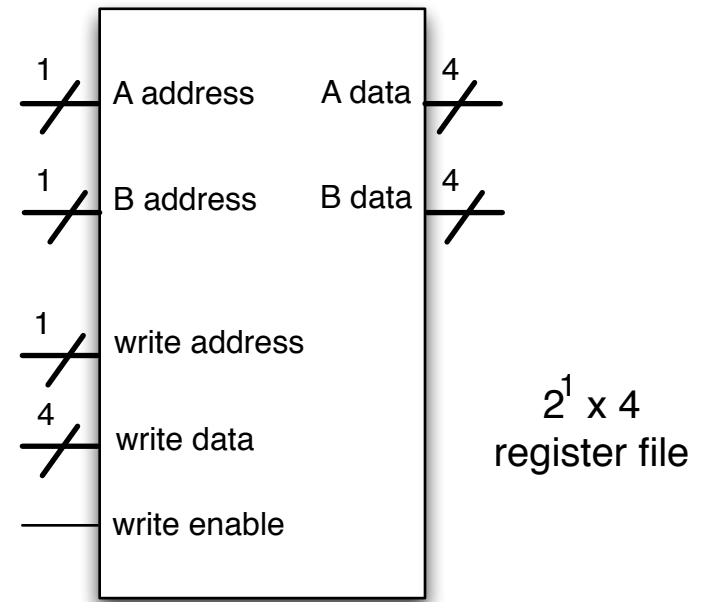
- **Let's consider a 2 word memory**
 - with 4-bit words



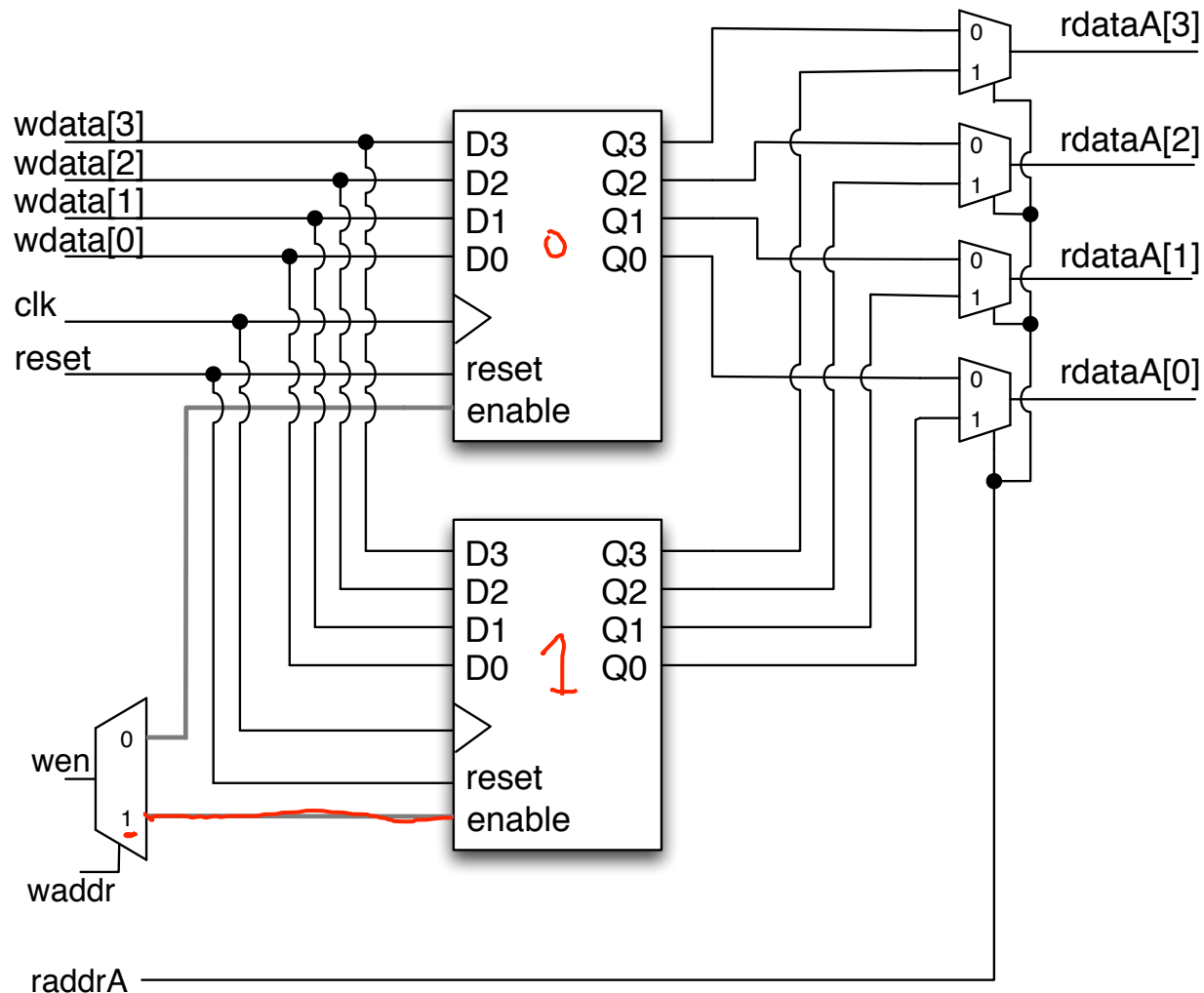2 x 4-bit register file (only 1 read port shown)



What does it do?

 

value stored

0	0x5
1	0x5 0xf