

Verilog Modules

```

module sc_block(s, c, a, b);
  output s, c;
  input a, b;
  wire w1, w2, not_a, not_b;

  // the "c" output is just the AND of the two inputs
  and a1(c, a, b);

  // the "s" output is 1 only when exactly one of the inputs is 1
  not n1(not_a, a);
  not n2(not_b, b);
  and a2(w1, a, not_b);
  and a3(w2, b, not_a);
  or o1(s, w1, w2);

endmodule // sc_block

```

Truth Table

a	b	s	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Draw a circuit diagram for the Verilog module above:

 
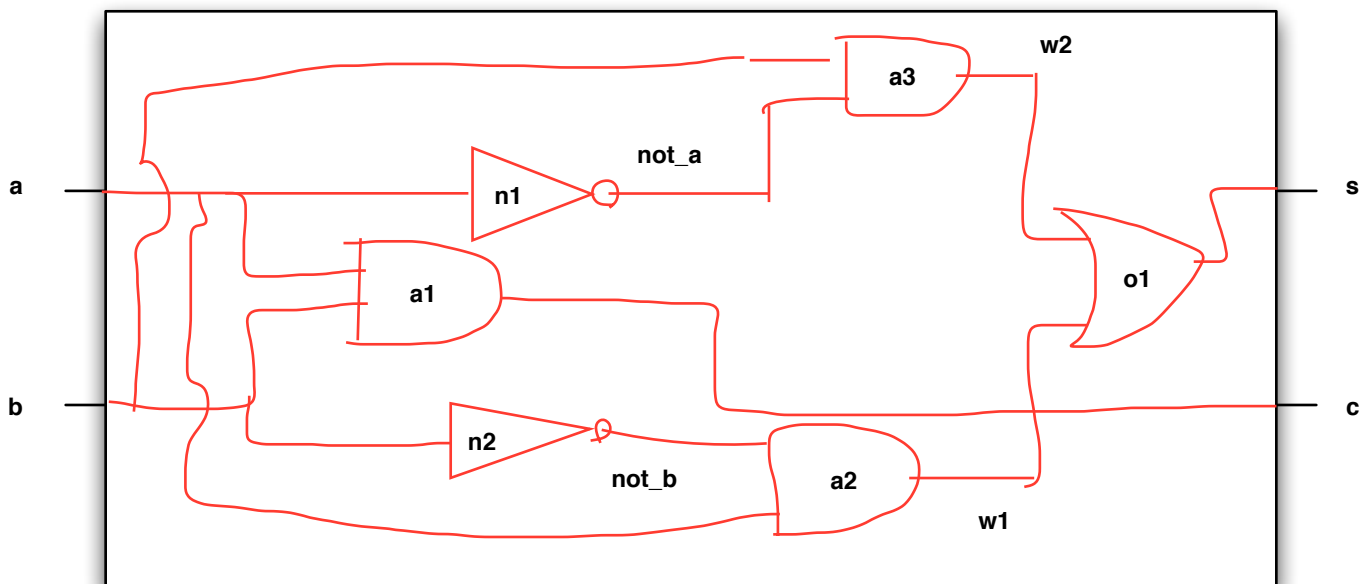


Figure 1. AND, OR, and NOT gates.

Hierarchical design: building modules from modules

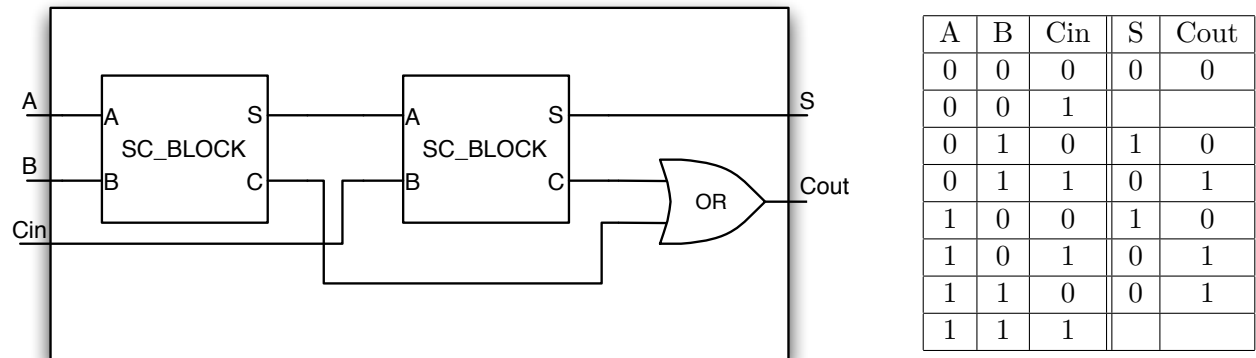


Figure 2. The `sc2_block`, which is implemented using `sc_block`, and its partially completed truth table.

Complete the truth table and write the Verilog for the `sc2_block` module: