



Boolean Algebra and Its Relation to Gates

An Introduction to CS233

233 in one slide!


- **The class consists roughly of 4 quarters:**
 1. You will build a simple computer processor
 2. You will learn how high-level language code executes on a processor
 3. You will learn why computers perform the way they do
 4. You will learn about hardware mechanisms for parallelism
- **We will have a SPIMbot contest!**
- **Section begins this week, so I must teach you something!**
 - More on class mechanics on Wednesday...

Today's lecture

- **Basic Boolean expressions**
 - Booleans
 - AND, OR and NOT
 - Expressing Boolean functions:
 - as **truth tables**
 - as mathematical **expressions**
 - as digital circuits made of **gates**
 - using **hardware description languages**

Computing: It is all just ones and zeros

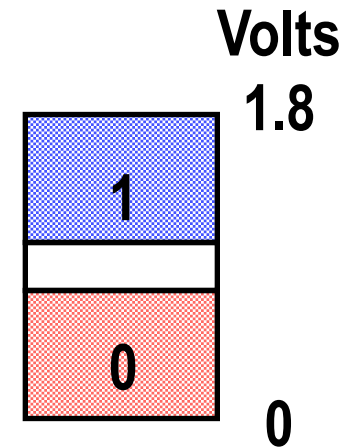
- Computers use voltages to represent information.
- For reliability and ease of design, however, we group ranges of voltages into two discrete, or digital, values: 1 and 0.
 - This two-valued domain is referred to as **BINARY**
 - Often **1** is used for **TRUE** and **0** for **FALSE**.
- Everything in digital computers is represented with ones and zeros
 - We'll show you how.



Boolean values

- If we think of our digital voltages as two *logical* values, **true** and **false**, we call these “Booleans”

- After the mathematician George Boole

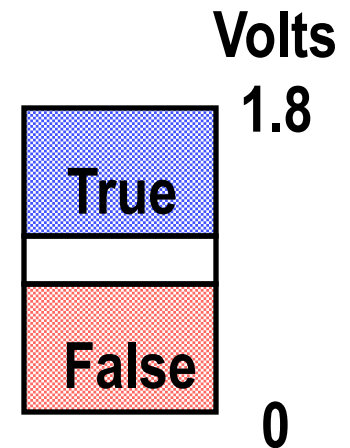

- For simplicity, we often still write digits instead:

- **1** is true
 - **0** is false

- Boolean algebra is the mathematics defined over this binary domain.

Boolean functions

- Just like in other mathematics, we can define functions:

$$y = f(x)$$

- The output is specified purely by the function & inputs
- Because there are a finite number (2) of boolean values...
 - There are a finite number of boolean functions
- For 1-input functions (e.g., $f(x)$) there are only 4 possible
 - (let's first see how to represent these...)

Truth tables

- A **truth table** shows all possible inputs & outputs of a function.
- Each input variable is either 1 or 0. (so are the outputs.)
 - Because there are only a finite number of values (1 and 0), truth tables themselves are finite.
 - A function with n variables has 2^n possible combinations of inputs.

x	y	z	$f(x,y,z)$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

1-input Boolean functions

$$y = f(x)$$

- A 1-input Boolean function has $2^1 = 2$ possible inputs:
- There are $2^{(\# \text{ of inputs})}$ possible functions
 - For each input, there are 2 possible outputs
 - The outputs are independent for each input (hence the multiplication)
- The 4 possible 1-input Boolean functions

x	f(x)
0	f(0)
1	f(1)

x	$f_0(x)$
0	0
1	0

x	$f_1(x)$
0	0
1	1

Buffer
/
Repeater

x	$f_2(x)$
0	1
1	0

x	$f_3(x)$
0	1
1	1

2-input Boolean functions

$$z = f(x, y)$$

- 4 possible inputs, 16 possible functions:

x	y	f0	f1	f2	f3	f4	f5	f6	f7	f8	f9	f10	f11	f12	f13	f14	f15
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

AND

OR

- We'll focus on 2 for now

Basic Boolean operations

- There are three basic operations for logical values.

Operation:

AND (product)
of two inputs

OR (sum) of
two inputs

NOT
(complement)
on one input

Expression

Notation:

xy , or $x \cdot y$

$x + y$

x' or \bar{x}

Truth table:

x	y	xy
0	0	0
0	1	0
1	0	0
1	1	1

x	y	x+y
0	0	0
0	1	1
1	0	1
1	1	1

x	x'
0	1
1	0

These are sufficient to implement any Boolean function

Boolean expressions (formally)

- Use these basic operations to form more complex expressions:

$$f(x,y,z) = (x + y')z + x'$$

- Some terminology and notation:

- f is the name of the function.
- (x,y,z) are the **input variables**, each representing 1 or 0. Listing the inputs is optional, but sometimes helpful.
- A **literal** is any occurrence of an input variable or complement. The function above has four literals: x , y' , z , and x' .

- **Precedences are important, but not too difficult.**

- NOT has the highest precedence, followed by AND, and then OR.
- Fully parenthesized, the function above would be kind of messy:

$$f(x,y,z) = (((x + (y'))z) + x')$$

Boolean expressions to Truth tables

- To compute a truth table given a Boolean expression:
 - Evaluate the function for every combination of inputs.

$$f(x,y,z) = (x + y')z + x'$$



$$f(0,0,0) = (0 + 1)0 + 1 = 1$$



$$f(1,0,1) = (1 + 1)1 + 0 = 1$$






x	y	z	f(x,y,z)
0	0	0	1
0	0	1	
0	1	0	
0	1	1	
1	0	0	1
1	0	1	
1	1	0	
1	1	1	
1	1	1	

a)	0
b)	1

Primitive logic gates

- Each of our basic operations can be implemented in hardware using a **primitive logic gate**.
 - Symbols for each of the logic gates are shown below.
 - These gates output the product, sum or complement of their inputs.

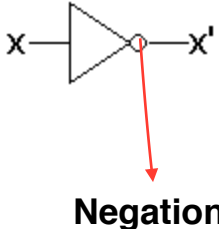	NOT (complement) on one input		
Operation:	AND (product) of two inputs	OR (sum) of two inputs	
Expression:	xy, or $x \cdot y$	$x + y$	x'
Logic gate:			

Boolean expressions to circuits

- Any Boolean expression can be converted into a **circuit** in a straightforward way.
 - Write a gate for each operation in the expression in precedence order.
 - We typically draw circuits with inputs on left and outputs on right.

$$(x + y')z + x'$$



Inputs

x

y


z

Output

$$(x + y')z + x'$$

Converting circuits to expressions

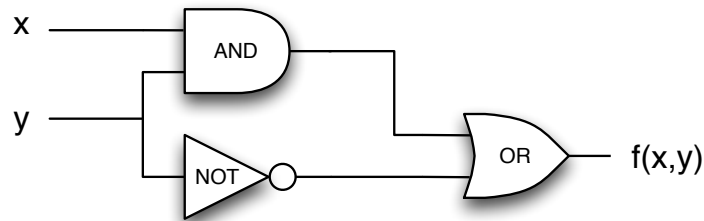- What Boolean expression does this circuit implement?




- a) $(x + y)y'$
- b) $x + y + y'$
- c) $xy' + y$
- d) $(xy) + y'$
- e) $(x+y)(x+y')$

Hardware Description Languages (HDL)

- **Textual descriptions of circuits**
 - (We're very good at manipulating text...)

A Circuit:

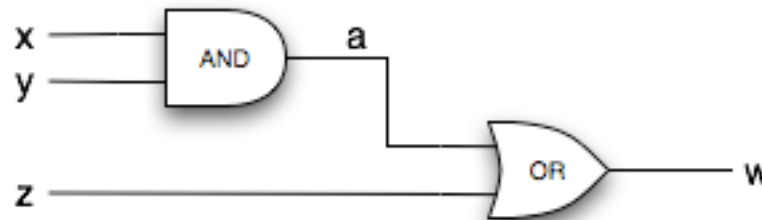


**Verilog
HDL Code:**

```
wire x, y, z, a, w;  
and a1(a, x, y);    // gatetype name(out, in1, in2);  
or o1(w, a, z);
```

- **Not like a normal programming language**
 - Each statement describes one or more gates and/or wires.

Boolean functions summary

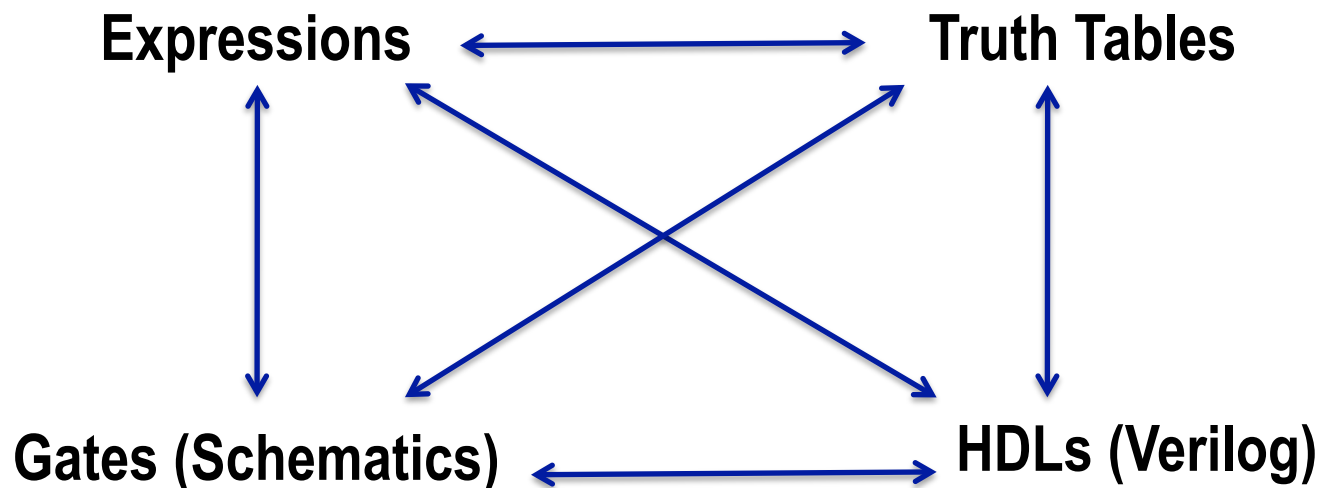- We can interpret high and low voltages as true and false.
- A Boolean variable can be either 1 or 0.
- AND, OR, and NOT are the basic Boolean operations.
- We can express Boolean functions in many ways:
 - Expressions, truth tables, circuits, and HDL code
 - These are different representations for equivalent things



Discussion Section starts this week!

- We'll introduce you to the tools designing, testing, and debugging digital logic circuits
 - Verilog
 - Waveform Viewers