

---

# Combinational Logic Design

# Today's lecture


- **Combinational Logic**
  - Different Representations of Boolean Functions (review)
- **How to design any circuit**
  - Write a truth table
  - Sum-of-Products implementation
  - Example
- **Other gates you should know about (XOR, NAND, NOR)**
- **Divide-and-Conquer design**

# Combinational Logic

- **Definition:** Boolean circuits where the output is a pure function of the present input only.
- **Circuits made up of gates, that don't have any feedback**
  - No feedback: **outputs** are not connected to **inputs**
  - If you change the inputs, *and wait for a while*, the correct outputs show up.
    - Real circuits have delays (more on this later)
- **Can be represented by Boolean Algebra**

# Four representations of Boolean functions

- Equivalent functionality

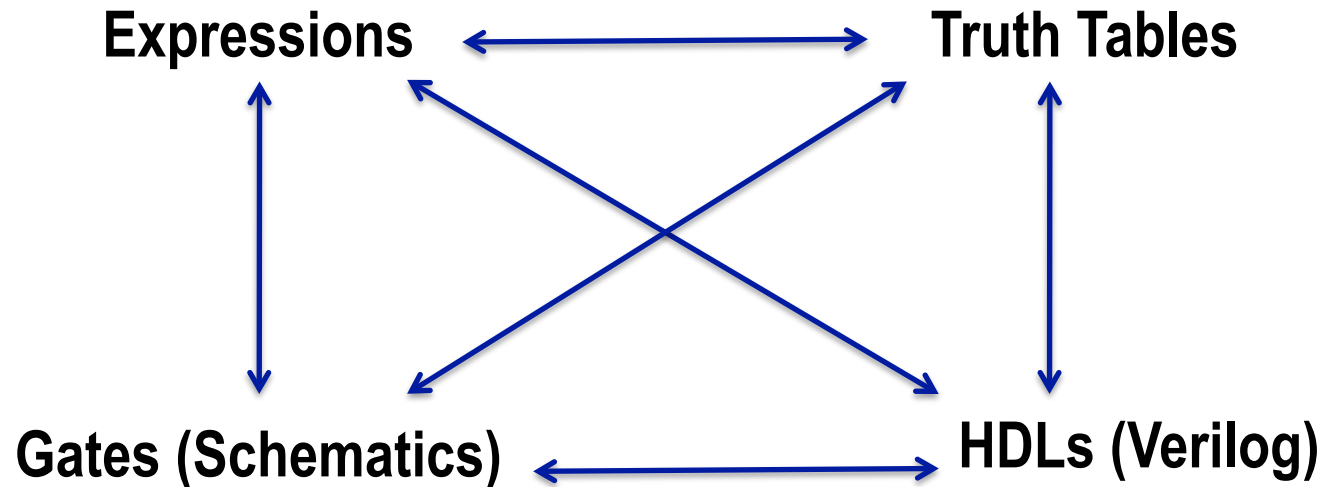

- Relatively mechanical to translate between these formats

# A fifth representation

## ■ An English description/specification

**Example:** A sandwich shop has the following rules for making a good (meat) sandwich:

- (1) All sandwiches must have at least one type of meat.
- (2) Don't put both roast beef and ham on the same sandwich.
- (3) Cheese only goes on sandwiches that include turkey.

Write a Boolean expression for the allowed combinations of sandwich ingredients using the following variables:

c = cheese

h = ham

t = turkey

r = roast beef

# English → Truth Table example

- **Most reliable method**

1. Write a truth table
2. Every row evaluating to 1 becomes a term
3. OR all the terms together

- **This will give an un-optimized expression**


- (we can write computer programs to optimize expressions)
  - (or better yet, use the ones that other people wrote...)
- (we can't write programs to design circuits for us.)

# Sum of Products (SOP) form

- A useful way to represent any Boolean expression
- A **sum of products (SOP)** expression contains:
  - only OR (sum) operations at the “outermost” level
  - Each term that is summed must be a product of literals

$$f(x,y,z) = y' + x'yz' + xz$$

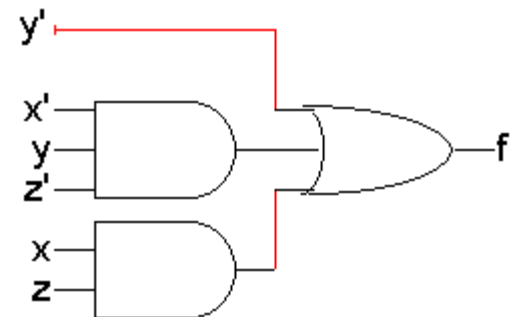- The advantage is that any sum of products expression can be implemented using a **two-level circuit**
  - literals and complements at “0th” level
  - AND gates at the first level
  - a single OR gate at the second level



# Truth tables to Boolean expressions

1. **For each row in truth table where output is 1**
  - Write a product term that is true for that set of inputs
    - And only for that set of inputs

x	y	z	f(x,y,z)
1	0	1	1



**$xy'z$**

- This product will include each terminal exactly once

2. **OR all the product terms together**

product-term1 + product-term2 + product-term3 + ...



# Truth table -> Boolean -> gates example

## Step 1. Write a truth table

### Rules:

- (1) must have at least one meat.
- (2) not both roast beef and ham.
- (3) cheese only if turkey.

**Ingredients:** c = cheese  
h = ham  
t = turkey  
r = roast beef

c	h	t	r	f(..)
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

a	b	c	d	e
0	0	1	0	0
1	0	1	0	0
1	1	0	1	1
1	1	0	0	1

## Step 2. Every 1 becomes a term

# Truth table -> Boolean -> gates example

## Step 1. Write a truth table

### Rules:

- (1) must have at least one meat.
- (2) not both roast beef and ham.
- (3) cheese only if turkey.

**Ingredients:** c = cheese  
h = ham  
t = turkey  
r = roast beef

c	h	t	r	f(..)	
0	0	0	0	0	
0	0	0	1	1	c'h't'r
0	0	1	0	1	c'h't'r'
0	0	1	1	1	c'h'tr
0	1	0	0	1	c'ht'r'
0	1	0	1	0	
0	1	1	0	1	c'htr'
0	1	1	1	0	
1	0	0	0	0	
1	0	0	1	0	
1	0	1	0	1	ch'tr'
1	0	1	1	1	ch'tr
1	1	0	0	0	
1	1	0	1	0	
1	1	1	0	1	chtr'
1	1	1	1	0	

## Step 2. Every 1 becomes a term





# Truth table -> Boolean -> gates example

Step 3. OR all the terms together

c	h	t	r	f(..)	
0	0	0	0	0	
0	0	0	1	1	$c'h't'r$
0	0	1	0	1	$c'h'tr'$
0	0	1	1	1	$c'h'tr$
0	1	0	0	1	$c'ht'r'$
0	1	0	1	0	
0	1	1	0	1	$c'htr'$
0	1	1	1	0	
1	0	0	0	0	
1	0	0	1	0	
1	0	1	0	1	$ch'tr'$
1	0	1	1	1	$ch'tr$
1	1	0	0	0	
1	1	0	1	0	
1	1	1	0	1	$chtr'$
1	1	1	1	0	
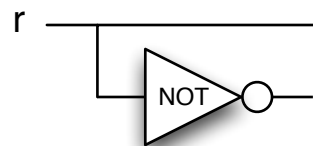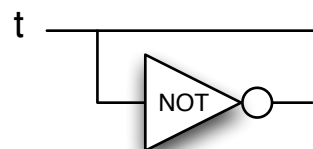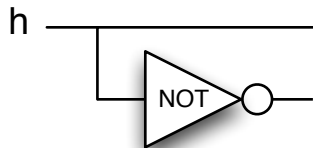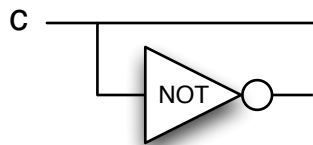
# Truth table -> Boolean -> gates example


$$c'h't'r + c'h't'r' + c'h't'r + c'ht'r' + c'htr' + ch't'r' + ch't'r + chtr'$$



— sandwich
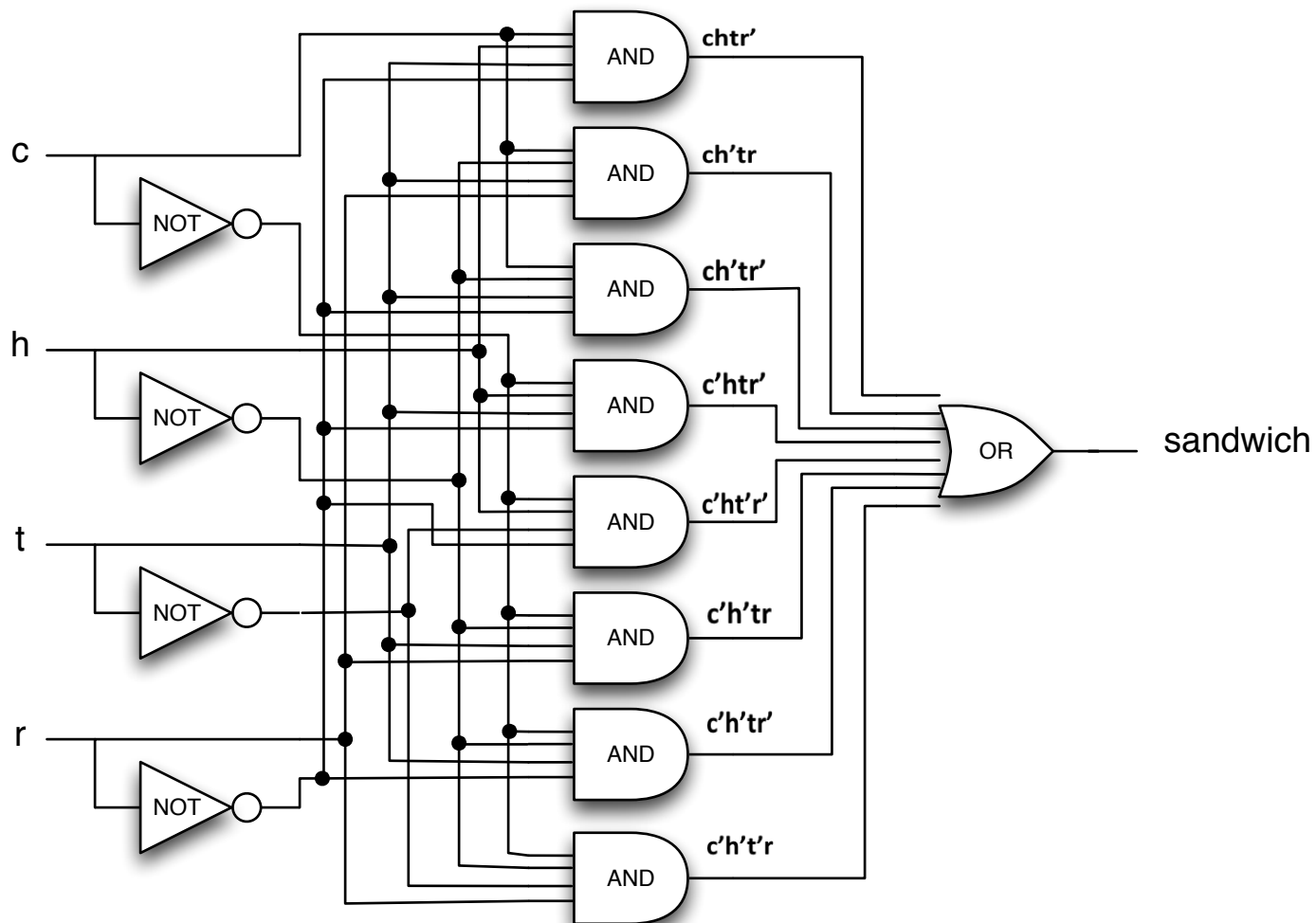
# Truth table -> Boolean -> gates example

$$c'h't'r + c'h't'r' + c'h't'r + c'ht'r' + c'ht'r' + ch't'r' + ch't'r + chtr'$$



# Three other notable 2-input functions

- Remember this table?

		<div>AND</div>							<div>OR</div>								
x	y	f0	f1	f2	f3	f4	f5	f6	f7	f8	f9	f10	f11	f12	f13	f14	f15
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

# Additional Boolean operations

Operation:

**NAND**  
(NOT-AND)

**NOR**  
(NOT-OR)

**XOR**  
(eXclusive OR)

Expressions:

$$(xy)' = x' + y'$$

$$(x + y)' = x'y'$$

$$x \oplus y = x'y + xy'$$


Truth table:

x	y	$(xy)'$
0	0	1
0	1	1
1	0	1
1	1	0

x	y	$(x+y)'$
0	0	1
0	1	0
1	0	0
1	1	0

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

Logic gates:

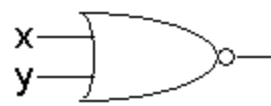

# XOR gates

- A two-input XOR gate outputs true when exactly one of its inputs is true:

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

$$x \oplus y = x'y + xy'$$

- XOR corresponds more closely to typical English usage of “either ... or,” *either of the two, but not neither nor both.*
- Several fascinating properties of the XOR operation:

---

$$x \oplus 0 = x$$

$$x \oplus 1 = x'$$

$$x \oplus x = 0$$

$$x \oplus x' = 1$$

---

$$x \oplus (y \oplus z) = (x \oplus y) \oplus z$$

[ Associative ]

$$x \oplus y = y \oplus x$$

[ Commutative ]

---



$$x \text{ XOR } y = x' \text{ XOR } y'$$

a) True


b) False

# Divide-and-Conquer Design

## ■ Consider the following problem

- You are building system to help avoid train collisions on subways.
- Each of the 28 segments of track:
  - Senses if there is a train on it ( $T = 1$ ) or no train ( $T = 0$ )
  - Has a red/yellow/green stoplight, where exactly 1 light is on at a time
    - The red light is on ( $R = 1$ ) if there is a train in the next segment
    - Otherwise, yellow is on ( $Y = 1$ ) if a train is 2 segments away
    - Else, green is on ( $G = 1$ )
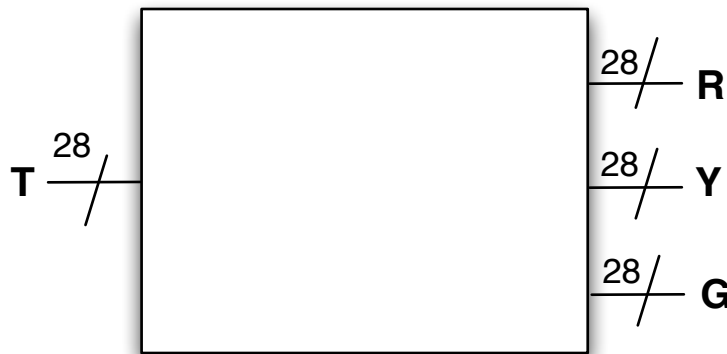
## ■ We could implement this as one big circuit.








Proximity  
sensor

---


**Why would that be a bad idea?**

# Divide-and-Conquer Design

- Instead build a module:

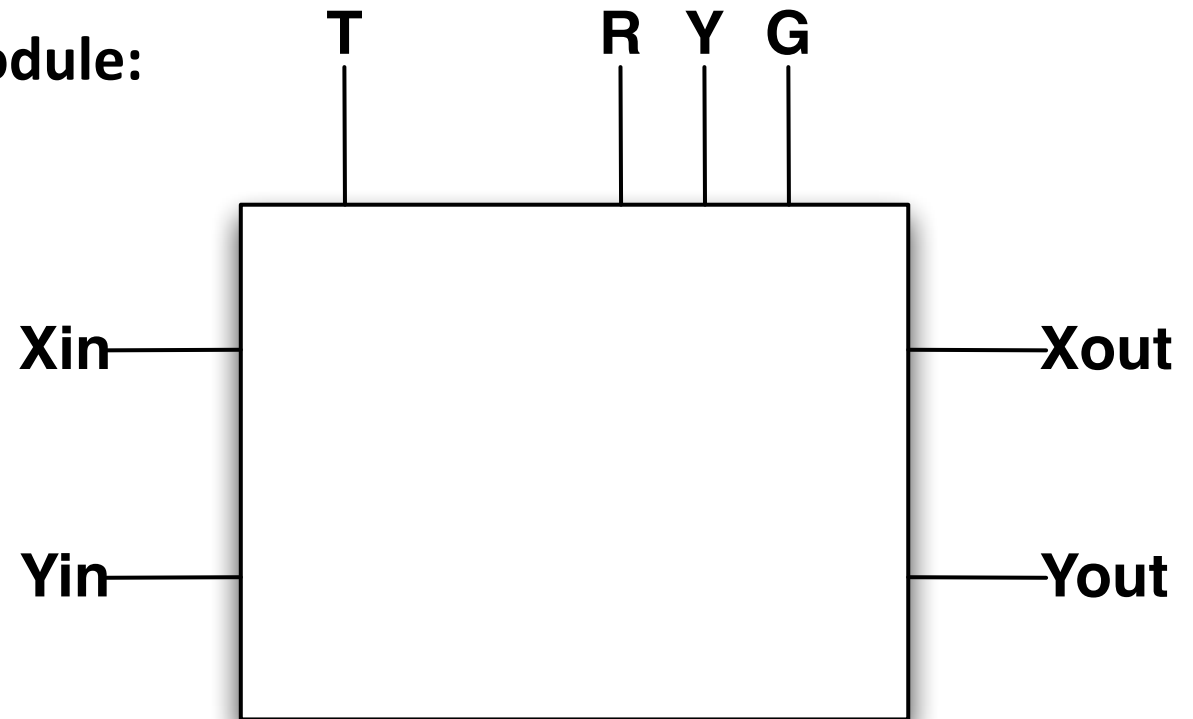

- And replicate:

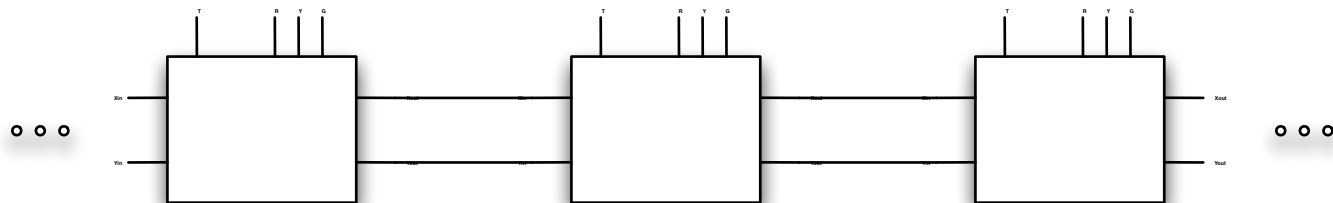



# What is $Y(Xin, Yin)$ ?



- a)  $Xin \oplus Yin$
- b)  $Xin + Yin'$
- c)  $Xin' + Yin$
- d)  $Xin \bullet Yin'$
- e)  $Xin' \bullet Yin$

# What is $G(X_{in}, Y_{in})$ ?



- a)  $X_{in}$  OR  $Y_{in}$
- b)  $X_{in}$  NOR  $Y_{in}$
- c)  $X_{in}$  AND  $Y_{in}$
- d)  $X_{in}$  NAND  $Y_{in}$
- e)  $X_{in}$  XOR  $Y_{in}$