



Propagation Delay and State


Today's lecture

- **Propagation Delay**
 - Timing diagrams.
 - Delay of ALU32
- **Storing State**
 - SR Latch
- **Synchronous Design**
 - Clocks
 - D Flip Flops

Propagation Delay


- Real gates don't switch instantaneously
 - There is a latency between when the input changes and the output changes.
 - We call this latency the propagation delay

- Consider an inverter:

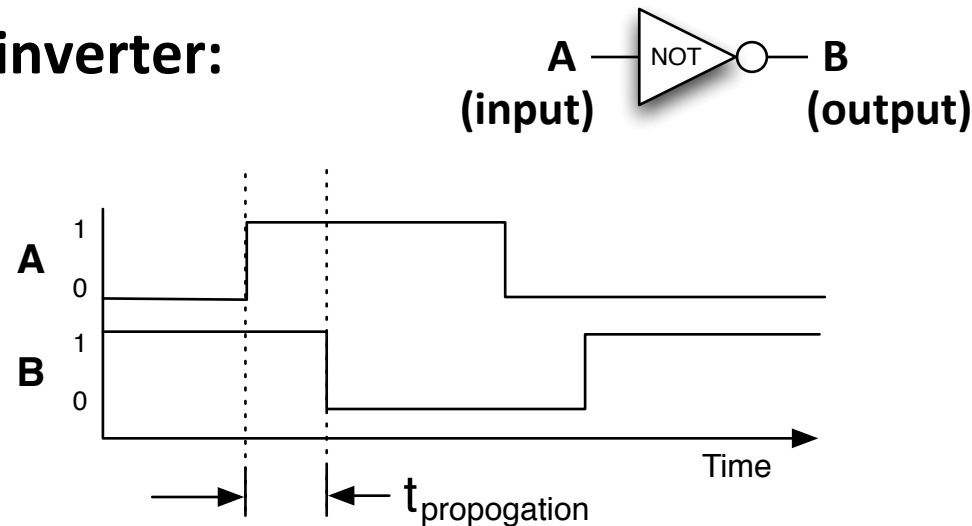


Ring Oscillator

 - What happens when you connect an odd number of inverters in a circle?



 If we connect even number of inverters,
the state would become stable and we can
store a bit inside



Timing analysis




- **In reality, timing is very complicated**
 - The delay from **x** to **z** can be different on an $0 \rightarrow 1$ transition than it is for a $1 \rightarrow 0$ transition.
 - The delay from **x** to **z** can differ from the delay from **y** to **z**.
 - The number of gates connected to the same output (the fanout), the longer it will take to switch.
 - Long wires between gates slow things down as well.
- **In this class, we'll use simplifying assumptions:**
 - Delay is a constant from any input to the output.
 - We'll ignore fanout and wire delay

Analyzing propagation delay of circuits

- **Assume:**

- Inverter: 20ps delay
- 2-input gate: 30ps delay
- 4-input gate: 50ps delay

 
- **Find longest paths from input to output**



In	Out	Delay
X	S	
Y	S	
Cin	S	
X	Cout	
Y	Cout	
Cin	Cout	


Computing the delay of alu32

 - What is likely to be the longest path through this circuit?
 - From any data input (A, B) bit to any output bit



- How long will it take?

Computing components from ALU1

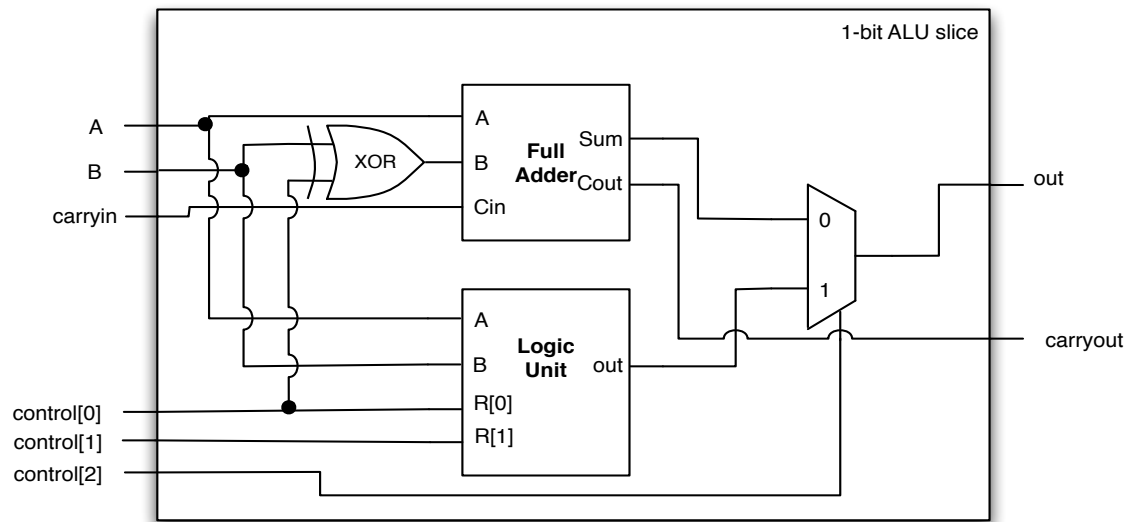

$$t_{\text{PropBCarryout}} + 30(t_{\text{PropCarryinCarryout}}) + t_{\text{PropCarryinOut}} =$$

**XOR
gate**

In	Out	Delay
A,B	out	30ps

**Full
Adder**

In	Out	Delay
A,B	Sum	
Cin	Sum	
A,B	Cout	
Cin	Cout	

**Logic
Unit**

In	Out	Delay
A,B	out	110ps
R	out	10ps

**2-to-1
Multiplexor**


In	Out	Delay
A,B	out	60ps
R	out	80ps

Thinking about ALU32's delay


- That is really bad. Really, really bad.
- Processors don't really implement ADDs this way
 - This is what is called a “ripple carry adder”
 - It has latency $O(n)$ where n is the # bits being added
- There are much smarter ways to handle carries
 - E.g., “carry lookahead adder” (Google it)
 - Has latency $O(\log_2(N))$ and only slightly larger
- But, we won't cover them in this class.

Rings of Inverters

 - We saw an odd number of inverters creates a ring oscillator:



 - What happens if you have an even number of inverters?




If we connect even number of inverters,
the state would become stable and we can
store a bit inside

Building a useful storage mechanism

- A memory should have at least three properties.

1. It should be able to hold a value. ✓
2. You should be able to *read* the value that was saved. ✓
3. You should be able to *change* the value that's saved. ✗

Cross-coupled inverters:

 

Set/Reset Latch (SR latch)

- **Cross-coupled NOR gates**

- Two inputs:

- **reset**: when 1, sets $Q=0$


- **set**: when 1, sets $Q=1$

- When **reset=set=0**, Q keeps its value

- *reset=set=1 causes bad things. Make sure this doesn't happen.*

- **This circuit has feedback, its outputs (Q , Q') are also inputs!**

 - Current values of Q , Q' depend on past values of Q , Q'



$$Q_{t=x} =$$

$$Q'_{t=x} =$$

Analyzing SR latch

$$Q_{t=x} = (\text{reset} + Q'_{t=x-1})'$$

$$Q'_{t=x} = (\text{set} + Q_{t=x-1})'$$

- **Case 1:** reset = set = 0 @ t = 0

$$Q_{t=1} =$$

$$Q'_{t=1} =$$

$Q_{t=0}$
 $Q_{t=0}$
 $Q_{t=0}$
 $Q_{t=0}$
 $Q_{t=0}$

- **Case 2:** reset = 1, set = 0

$$Q_{t=1} =$$

$$Q'_{t=1} =$$

- **Case 3:** reset = 0, set = 1

$$Q_{t=1} =$$


$$Q'_{t=1} =$$

Timing diagram of an SR Latch

Initialized to $Q=0$

$$Q_{t=x} = (\text{reset} + Q'_{t=x-1})'$$

$$Q'_{t=x} = (\text{set} + Q_{t=x-1})'$$

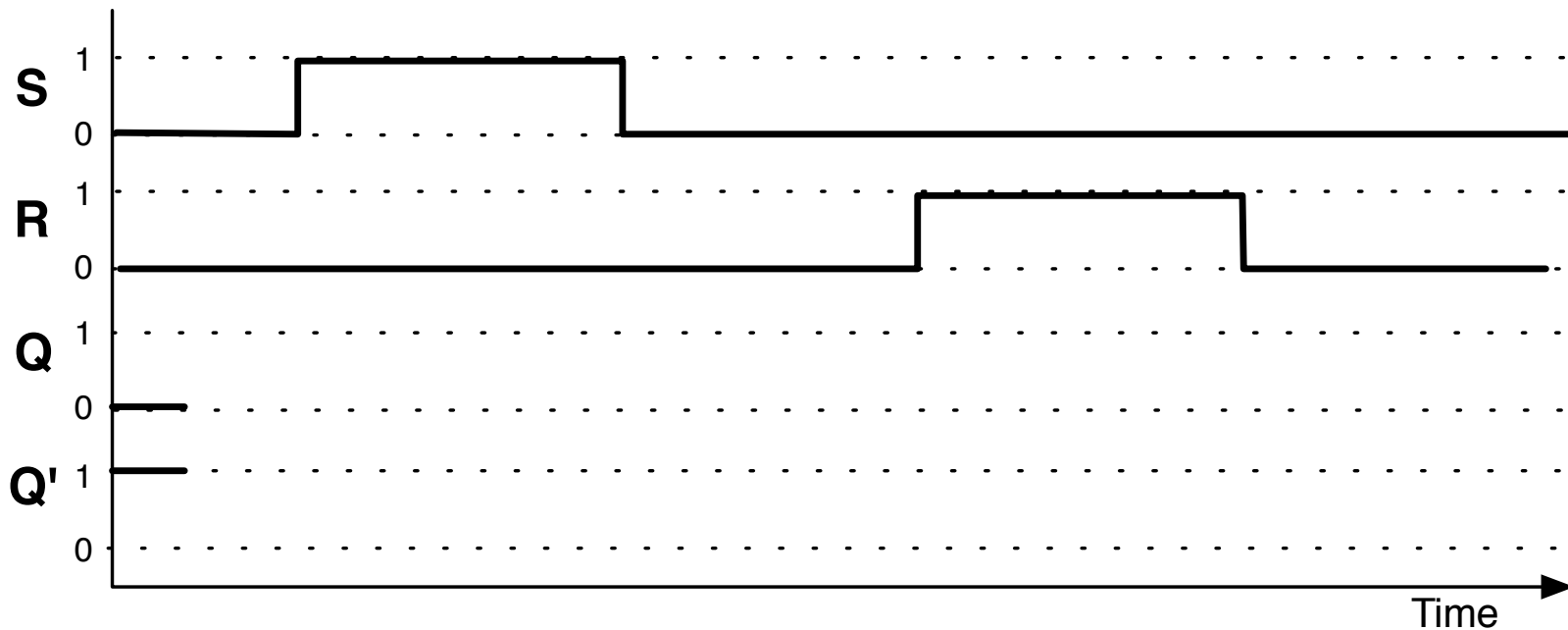

SR Latches are a useful storage mechanism

- An SR latch provides the three features:

- It holds its value
- We can read its value
- We can change its value

S	R	Q
0	0	No change
0	1	0 (reset)
1	0	1 (set)

- We call the data stored (Q) the **state** of the latch.

- 1 bit of information is stored

- We the behavior as a **state table**, which explicitly shows that the *next* values of Q and Q' depend on their *current* values, as well as on the inputs S and R.

Inputs		Current		Next	
S	R	Q	Q'	Q	Q'
0	0	0	1	0	1
0	0	1	0	1	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0

Aside: SR Latches are not combinational circuits

- In the 2nd lecture we defined **Cominational Logic** as:
Boolean circuits where the output is a pure function of the present input only.

- Below we can see this doesn't hold for the SR Latch
 - When $S = R = 0$ we can have two different outputs


- The SR Latch is a **Sequential** circuit

The outputs of a **sequential circuit** depend on not only the inputs, but also the **state**, or the current contents of some memory.

Inputs		Current		Next	
S	R	Q	Q'	Q	Q'
0	0	0	1	0	1
0	0	1	0	1	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0


Synchronous Design

 - *The easiest (and most common) way to build computers*
- All state elements get updated at the **same time**
 - Using a clock signal
- **Clock signal**
 - A square wave with a **constant period**




- **We always update state at the same point in wave**
 - E.g., the rising edge

Synchronous Design, cont.

 


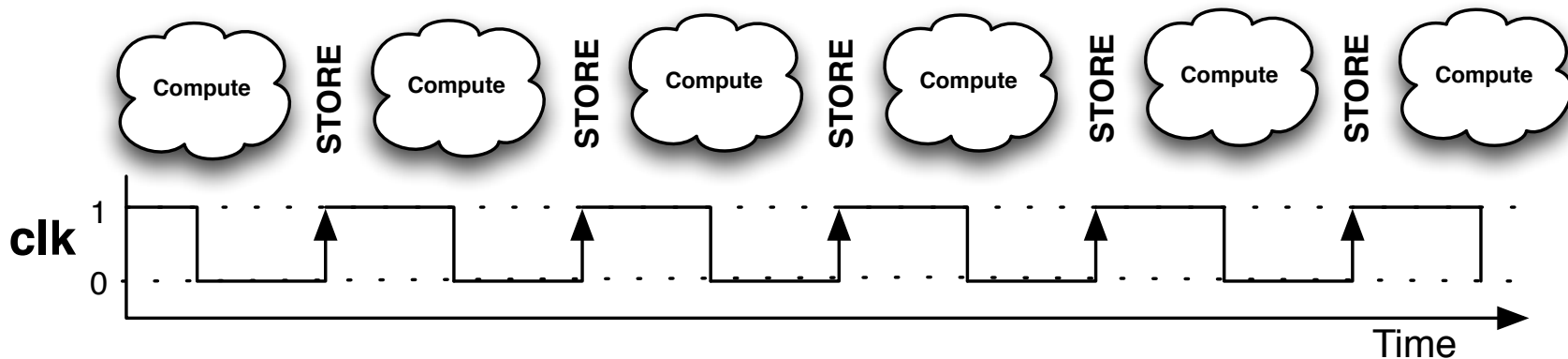
- Alternate between computation and updating state.



The state element that we really want...


■ The D flip flop

  - Holds 1 bit of state
 - Output as Q.
- Inputs
 - Copies D input into state on rising edge of clock.



Implementing the D-type Flip Flop


- Remember the SR Latch?

 

S	R	Q
0	0	No change
0	1	0 (reset)
1	0	1 (set)

- We're going to two special kinds of latches.
 - SR Latch with enable
 - D Latch with enable


SR Latch with Enable

 

enable	S	R	S'	R'	Q
0	x	x	1	1	No change
1	0	0	1	1	No change
1	0	1	1	0	0 (reset)
1	1	0	0	1	1 (set)
1	1	1	0	0	Avoid!

- Take SR Latch, make it ignore input when enable = 0


D-latch with Enable

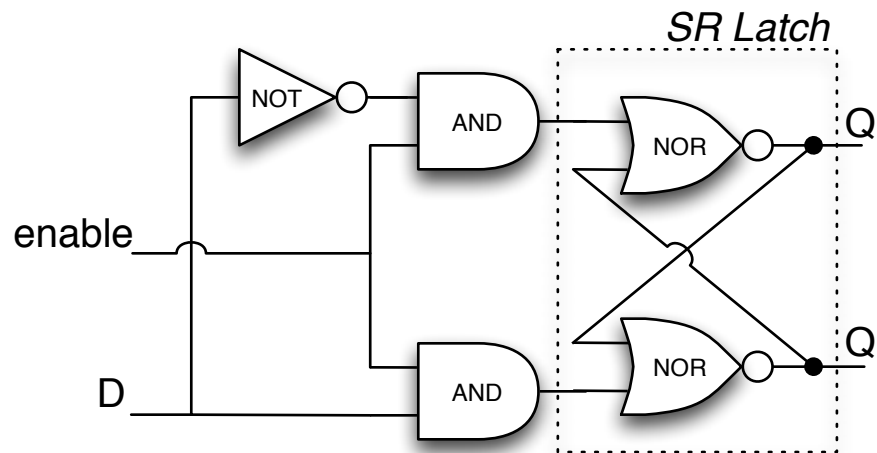

Enable	D	Q
0	X	No change
1	0	0
1	1	1

- Take SR Latch with Enable, make reset = !set
 - State get set to whatever D is.

The D Flip Flop

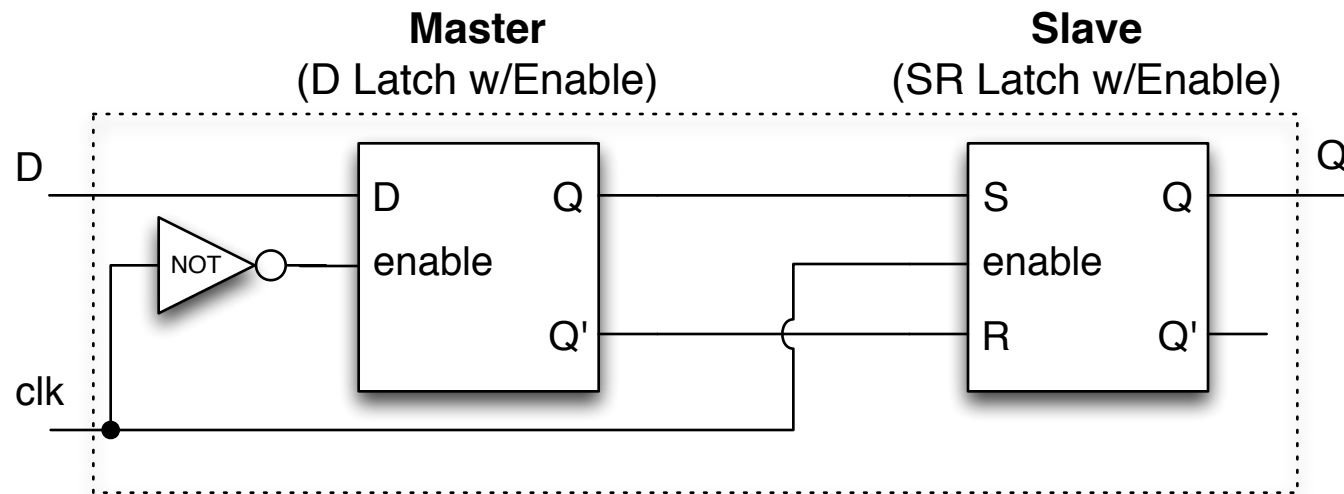

- **Only one of the latches is enabled at a time**
 - When $\text{clk}=0$, the master is transparent; slave holds its value
 - When $\text{clk}=1$, the master holds its value; slave transparent
- **On rising edge, value at master's input passed to slaves output.**